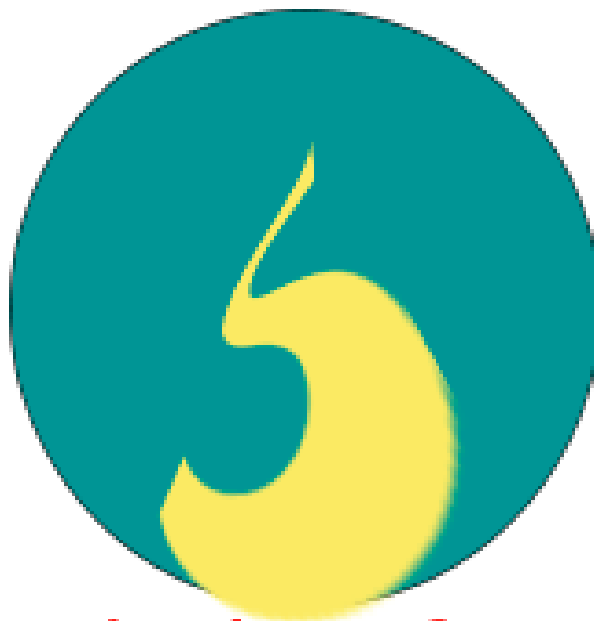


**TECHNICAL ANALYSIS – CIRCUIT  
PARAMETER DETERMINATION  
WITH OPTOCOUPLER**



**Think Perfect**

**Selva LLC**

**Consultant – Process Automation, AutoCAD Electrical,  
Engineering Design**

**Selva LLC: 330, Springwell Lane, Alpharetta, GA 30004.**

**USA.PH: (770) 337-5380**



## Contents

1. Introduction .....	1
2. Circuit Diagram and Description .....	1
3. Schematic Representation .....	2
3.1 Key Observations .....	2
3.2 Methodology .....	2
4. Derivation of Equations .....	2
4.1 Experimental Measurements and Equation Formulation .....	3
4.1.1 First Test Case .....	3
4.1.2 Second Test case .....	3
4.1.3 Third Test Case .....	4
5. Solving for Circuit Parameters .....	5
6. Detailed Analysis of Equivalent Resistance Equations .....	6
6.1 Understanding the Parallel resistance Concept .....	6
6.1.1 First Measurement Case Analysis .....	6
6.1.2 Second Measurement Case Analysis .....	7
6.1.3 Establishing the System of Equations .....	8
7. Equation Solving Methodology .....	8
8. Results .....	10



## Technical Analysis - Circuit Parameter Determination with Optocoupler

### 1. Introduction

This study presents a detailed analysis of a resistive circuit incorporating an optocoupler diode ( $R_d$ ). The objective is to derive the values of resistors  $R_1$ ,  $R_2$  and the dynamic resistance of the optocoupler ( $R_d$ ) using experimental voltage and current measurements.


The analysis employs Kirchhoff's Voltage Law (KVL) and Ohm's Law to derive and solve a system of equations. The nonlinear behaviour of  $R_d$  necessitated solving a system of equations for accurate parameter extraction.

### 2. Circuit Diagram and Description

- The circuit under study consists of a variable DC power supply set to 24V, though the actual measured voltages vary due to load conditions.
- A resistor  $R_1$  is connected in series with a parallel combination of another resistor  $R_2$  and an optocoupler diode ( $R_d$ ).
- The optocoupler introduces a nonlinear resistance that changes with the current flowing through it, making the circuit's analysis more complex than a purely resistive network.
- The voltage across the parallel branch ( $R_2 || R_d$ ) is measured and the total current through  $R_1$  is recorded for each test case.
- Since, the optocoupler's resistance is not constant, the effective resistance of the parallel combination varies with the applied current.
- This variability necessitates a systematic approach to derive the values of  $R_1$ ,  $R_2$  and  $R_d$  using multiple measurements to account for the nonlinear effects.



## 3. Schematic Representation

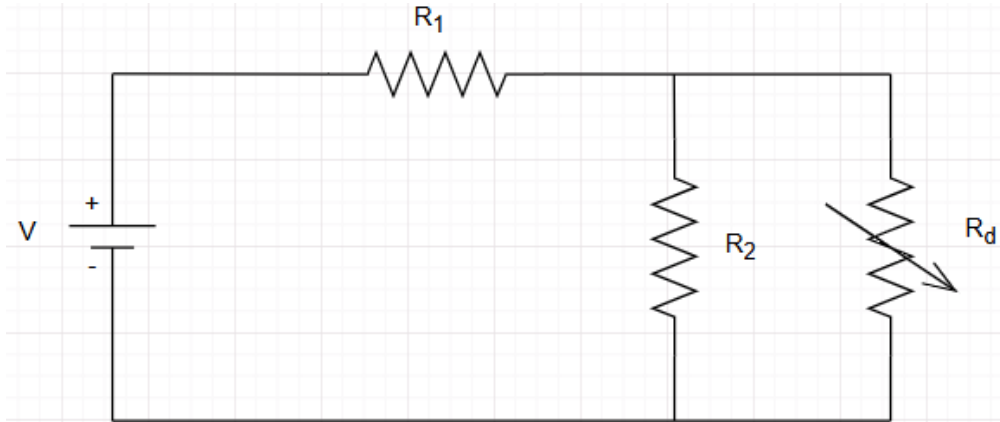

### 3.1 Key Observations

- The voltage across the circuit varies with current due to the nonlinear behaviour of  $R_d$
- Multiple test cases provide voltage (V) and current (I) readings, allowing us to derive  $R_1$ ,  $R_2$  and  $R_d$

### 3.2 Methodology

We apply Kirchhoff's Voltage Law (KVL) and Ohm's Law to the series-parallel network. The parallel relation used to express the node branch. Equations for each test case are set up and solved to estimate at the respective operating points

## 4. Derivation of Equations

- Using Kirchhoff's Voltage Law (KVL), the general equation for the circuit is,

$$V = IR_1 + I_{R2}R_2$$

Where,

V = Supply Voltage

I = Total Current through  $R_1$



$I_{R2}$  = Current through  $R_2$

$R_1$  &  $R_2$  = Resistance


## 4.1 Experimental Measurements and Equation Formulation

- Three distinct test cases were conducted, each providing a unique set of voltage and current readings.
- These measurements are used to construct a system of equations that describes the circuit's behaviour under different conditions.

### 4.1.1 First Test Case:

Voltage = 22.58 V

Current = 2.18 mA

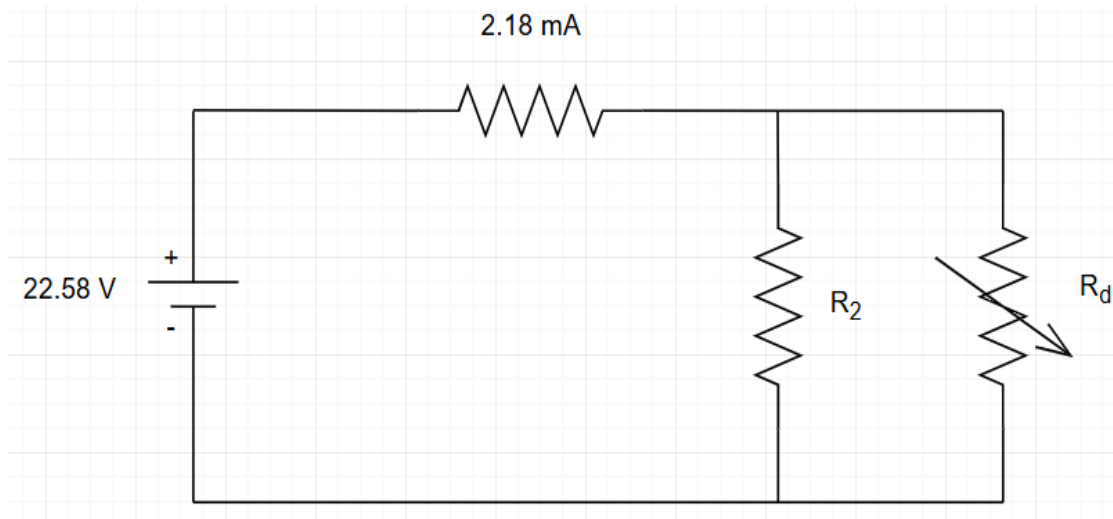

The equation derived is


$$22.58 = 2.18R_1 + I_{R2}R_2 \quad \dots\dots\dots (1)$$

Here,  $I_{R2}$  represents the current flowing through  $R_2$ .

### 4.1.2 Second Test Case:

Voltage = 18 V

Current = 0.9 mA

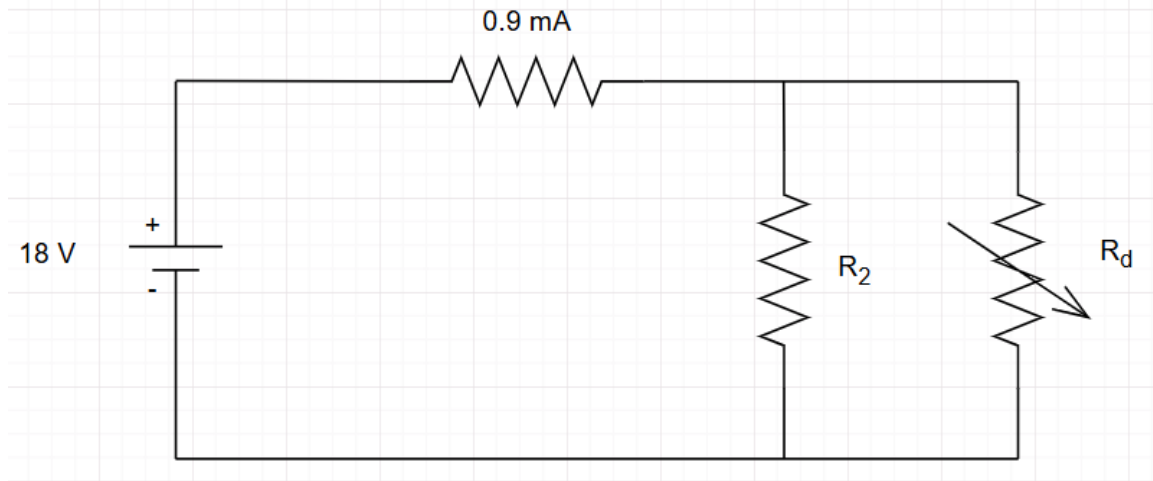


The corresponding equation is

$$18 = 0.9R_1 + I_{R2}R_2 \quad \dots\dots\dots (2)$$

### 4.1.3 Third Test Case:

Voltage = 31.2 V

Current = 4.8 mA

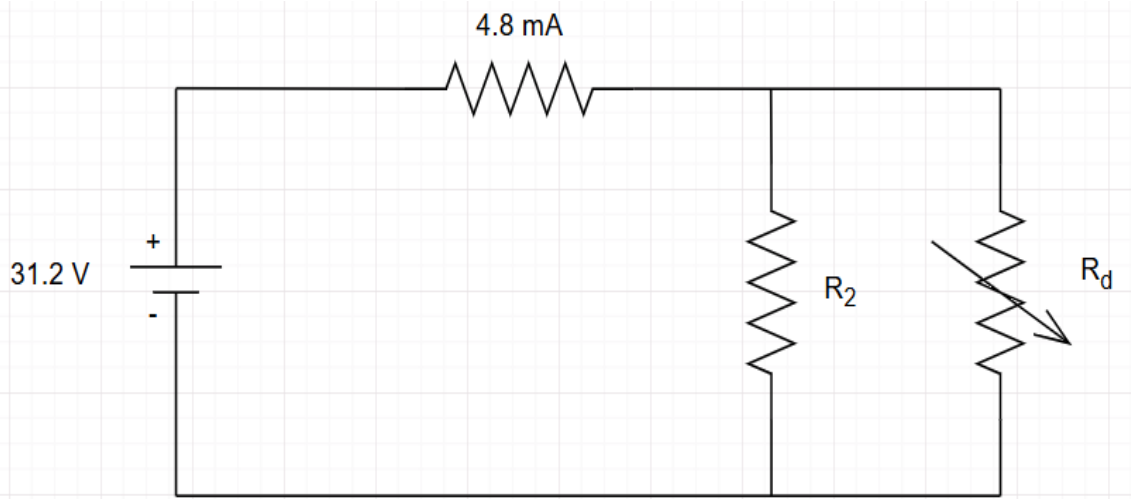

The equation becomes,

$$31.2 = 4.8R_1 + I_{R2}R_2 \quad \dots\dots\dots (3)$$

*These equations are solved simultaneously to isolate and determine the values of R1, R2 and Rd.*



## 5. Solving for Circuit Parameters

### Step 1: Determining $R_1$

- By subtracting the second equation from the third, the term  $I_{R_2}R_2$  cancels out, allowing us to solve for  $R_1$

$$31.2 - 18 = (4.8 - 0.9) R_1$$

$$13.20 = 3.9 R_1$$

$$R_1 = \frac{13.20}{3.9} = 3.385 \text{ k}\Omega$$

$$\mathbf{R_1 = 3.385 \text{ k}\Omega}$$

### Step 2: Calculating $I_{R_2}R_2$

- Substituting  $R_1 = 3.385 \text{ k}\Omega$  back into the second equation yields

$$18 = (0.9)(3.385) + I_{R_2}R_2$$

$$I_{R_2}R_2 = 18 - 3.0465 = 14.95 \text{ V}$$

$$\mathbf{I_{R_2}R_2 = 14.95 \text{ V}}$$

- Similarly, using the third equation

$$31.2 = (4.8)(3.385) + I_{R_2}R_2$$

$$I_{R_2}R_2 = 31.20 - 16.248 = 16.24 \text{ V}$$

$$\mathbf{I_{R_2}R_2 = 16.24 \text{ V}}$$

### Step 3: Resolving Discrepancies in $R_2$

- The value of  $R_2$  appears inconsistent when calculated from different test cases due to the influence of  $R_d$ . For instance,

From the second test case

$$\mathbf{R_2 = \frac{14.95}{0.9} = 16.61 \text{ k}\Omega}$$



From the third test case

$$R_2 = \frac{16.24}{4.8} = 3.383 \text{ k}\Omega$$

*This discrepancy arises because the effective resistance of the parallel combination  $R_2 || R_d$  changes with current, highlighting the nonlinearity introduced by the optocoupler.*

## 6. Detailed Analysis of Equivalent Resistance Equations

### 6.1 Understanding the Parallel Resistance Concept

The fundamental challenge in analysing this circuit lies in properly accounting for the parallel combination of resistor  $R_2$  and the optocoupler diode resistance  $R_{eq}$  is always less than either individual resistance.

This relationship is mathematically expressed through the standard parallel resistance formula:

$$R_{eq} = \frac{R_2 R_d}{R_2 + R_d}$$

In the circuit, this parallel combination forms the lower portion of a voltage divider, with  $R_1$  as the upper resistor

#### 6.1.1 First Measurement Case Analysis

From the second experimental measurement, we obtained an equivalent parallel resistance of 16.61 k $\Omega$ . This given first key equation

$$16610 = \frac{R_2 R_d}{R_2 + R_d}$$

When we rearrange this equation to eliminate the denomination, we get

$$16610(R_2 + R_d) = R_2 R_d$$





*This represents a nonlinear relationship between  $R_2$  and  $R_d$ , making it impossible to solve for either variable independently. The equation tells us that the product of the resistances equals 16610 times their sum. This form is particularly useful because it preserves the fundamental relationship while preparing the equation for simultaneous solution with another measurement.*

### 6.1.2 Second Measurement Case Analysis

The third experimental measurement yielded a different equivalent resistance of 3.383 kΩ.

However, we must recognize that the optocoupler’s resistance likely changed between measurements due to different operating currents.

*To account for this, here introduce a scaling factor  $x$  (calculated as 0.20 from the ration of the equivalent resistance)*

$$x = \frac{3383}{16610}$$

$$x = 0.20 \dots\dots\dots (4)$$

That related the two operating conditions. This gives second key equation

$$3383 = \frac{R_2 \times R_d}{R_2 + x R_d}$$

Substituting,  $x = 0.20$  and rearranging similarly gives

$$3383 = \frac{R_2 \cdot 0.20 R_d}{R_2 + 0.20 R_d}$$

*This equation now relates the same physical resistors but under different operating conditions, captured through the scaling of  $R_d$*

When we rearrange this equation to eliminate the denomination, we get



$$3383(R_2 + 0.20 R_d) = R_2 0.20 R_d$$

### 6.1.3 Establishing the System of Equations

Now, we have two properly formatted equations

$$16610(R_2 + R_d) = R_2 R_d \dots\dots\dots (5)$$

$$3383(R_2 + 0.20 R_d) = R_2 0.20 R_d \dots\dots\dots (6)$$

*This system of nonlinear equations presents a mathematical challenge because the variables  $R_2$  and  $R_d$  appear in both additive and multiplicative forms. The solution approach involves strategic manipulation to eliminate one variable at a time.*

## 7. Equation Solving Methodology

To solve this system, we employ the following steps:

### Step 1: Expand Both Equations

- Equation 5 becomes

$$16610 R_2 + 16610 R_d = R_2 R_d \dots\dots\dots (7)$$

- Equation 6 becomes

$$3383 R_2 + 676.6 R_d = R_2 0.20 R_d \dots\dots\dots (8)$$

### Step 2: Normalize the Equation

*Here noticed that both equations contain the  $R_2 R_d$  term. To facilitate elimination, multiply the equations to make these terms compatible*

- Multiply Equation 7 by 3383:

$$56191630 R_2 + 56191630 R_d = 3383 R_2 R_d \dots\dots\dots (9)$$

- Multiply Equation 8 by 16610:

$$56191630 R_2 + 11238326 R_d = 3322 R_2 R_d \dots\dots\dots (10)$$



### Step 3: Subtract to Eliminate Terms

- Subtracting the modified Equation 9 from the modified equation 10  
$$(56191630 R_2 - 56191630 R_2) + (56191630 R_d - 11238326 R_d)$$

$$= (3383 R_2 R_d - 3322 R_2 R_d)$$

- This simplifies to,

$$44953304 R_d = 61 R_2 R_d$$

### Step 4: Solve for $R_2$

- Divide both sides by  $R_d$  (assuming  $R_d \neq 0$ ) to get

$$44953304 = 61 R_2$$

Therefore:

$$R_2 = \frac{44953304}{61}$$

$$R_2 = 736939.41 \Omega$$

### Step 5: Back – Substitute to Find $R_d$

- Using Equation 8 with the known  $R_2$  value

$$(3383)(736939.41) + 676.6 R_d = (736939.41)(0.20) R_d$$

Expanding:

$$2493066024.03 + 676.6 R_d = 147387.882 R_d$$

Rearranging:


$$2493066024.0 = (147387.882 - 676.6) R_d$$

$$2493066024.0 = 146711.282 R_d$$

Solving:

$$R_d = \frac{2493066024.03}{146711.282}$$

$$R_d = 16993.0082 \Omega$$

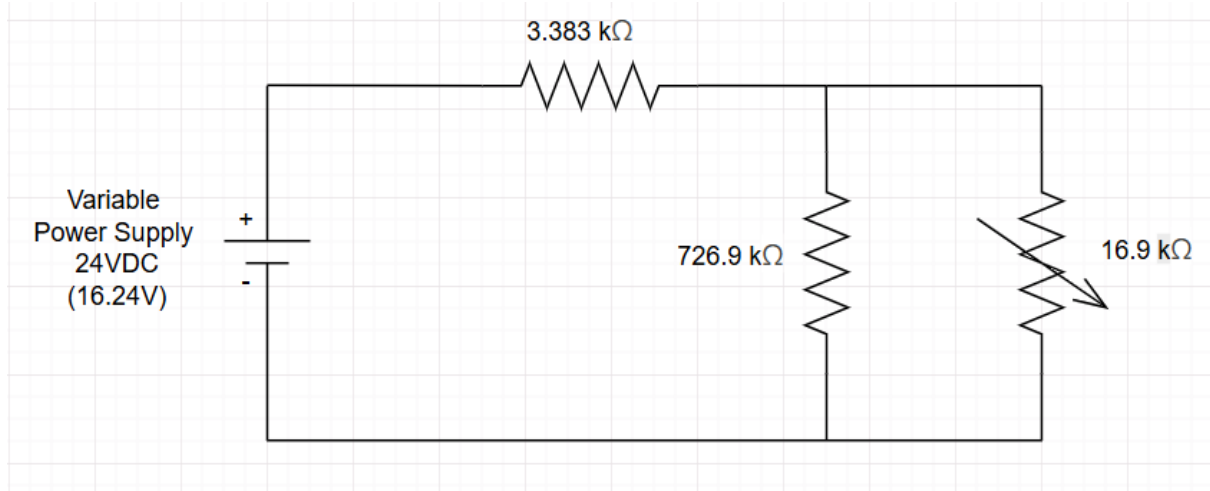

## 8. Results

Solving the system shows that  $R_d$  changes between cases, consistent with optocoupler behaviour. Small discrepancies in derived values between test cases are expected and reflect the operating-point dependence of  $R_d$ . Where needed, values can be linearized around a nominal current for design use.